Basic Electronics Course – Part 1

Simple Projects using basic components







Demo 1: A basic circuit – Lighting a globe with a battery

- Using 9v battery & Light Globe with leads Image 2. Hold one lead on the Positive terminal on top of the Battery [marked +ive]
- Hold the other lead on the Negative Terminal [marked -ive]
- Light Globe will light
- **That is a basic circuit** –power is running from one battery terminal through the leads & globe to the other battery terminal the circuit is complete and the light glows
- If you break the circuit.... lift one of the leads off the battery the light WILL NOT glow
- **Current must be flowing in a complete 'loop'** what stops a circuit operating? Flat battery, faulty globe, bad connection, a short circuit (e.g. plastic wire covering breaks & wires touch, wire broken inside of plastic
- **Electronic equipment is basically small individual circuits** Using many smaller circuits together simply makes a more complicated machine or device



Image 3. See "Note 1" on breadboard



Demo 2: Light Globe on Breadboard

- How is a Breadboard Constructed? See Note1 Read the Note and compare your breadboard
- Using a 9v battery: Attach the Battery cap with leads
- Push Red battery lead into a hole on Red +ive rail line on Breadboard
- Push Black battery lead into a hole on the Blue -ive rail line. The Board now has power
- Using a jumper lead. Push one end into a hole on the Red +ive rail line. Push other end into any short cross-row of holes That puts +Positive power to that short cross-row
- Use another jumper lead. Push one end into a hole on the Blue –ive rail line. Push other end into a hole on a short cross-row of holes on 'other side' of board –That completes -Negative power link
- The board has power but no components in the centre to complete a 'loop'
- Using a Globe with leads. Push one end into any hole in the same row that has the +ive jumper & push the other Globe Lead into any hole on the -ive jumper cross-row.
- Note <u>Image3</u> The Globe leads span across the dividing line of the breadboard and each lead is in a row that has either +ive or –ive power so the power Loop is now complete
- Light Globe will light if not. Check the line of 'power' does it flow from one line to the next? Is it a complete 'loop'? Are the jumper ends and the globe-lead ends cross-rows with +ive & -ive power leads?
- Current must be flowing in a complete 'loop' or else the Globe will not light

Demo 3: Add a Diode to Globe circuit on Breadboard

- Continuing from Demo 2 MOVE one Globe lead On the +ive side of the board, move lead to another Cross-Row breaking the power 'loop' [move it down a couple of cross-rows]
- Add a small, low voltage, low current diode in *Series with the Globe [see last 'dot'point]
- Note the Diode has one end marked +ive and the +ive leg is longer
- Push +ive Diode leg into a hole on the same Cross Row as the +ive power jumper lead
- Push the other end into any hole in the same Cross-Row as the moved Globe lead
- What is demonstrated? A Diode only passes current in one direction ie with diode in the correct way, the globe lights, if the diode is reversed, globe not light
- **Check this out:** Connect the diode back the correct way, note the Globe lights, NOW reverse the battery (polarity) and note the Globe will not light
- What use is a Diode? It protects components: If the globe was a sensitive electronic component that would fail if it was accidently connected "reverse polarity", we've demonstrated that a Diodes provide reverse polarity protection to that sensitive electronic component (or our globe)
- * "In series" means it follows end to end with the Light Globe



Demo 4: Piezo Buzzer on Breadboard

- Continuing from Demo 3 REMOVE the Diode & Light Globe take Globe & Diode out of the circuit
- Add a small 12Volt Piezo Buzzer Note Buzzer has one side marked +ive. and that +ive leg is longer
- Push +ive Buzzer leg into a hole on the same Cross Row as the +ive power jumper lead
- Push the other leg into any hole in the same Cross-Row as the -ive power jumper lead
- Buzzer legs are <u>spanning the gap in the board with one leg in each +ive and –ive Cross-Rows</u>
 power loop is complete
- When the Circuit is complete the Buzzer will sound and won't stop until a wire is removed from the board to 'break' the circuit.
- Buzzer goes Off and On as final wire is pushed In or Taken Out of the Circuit
- What is demonstrated? That a small 12V Piezo Buzzer <u>or any small</u> motor or relay [coil] could be used in a simple circuit instead of the light globe.

Demo 5: Introducing a Light Emitting Diode [LED]

- Connect 9v battery leads to Red+ & Blue- rail lines on Breadboard
- Use jumper leads to power <u>2 different Short Cross-Row of holes</u> 1 row +ive & 1 row -ive
- **Don't insert LED** until a Resistor is in Series with LED See Note 2 Reduce Voltage to Protect LEDs
- Using 3300hm Resistor Push 1 'leg' into a hole <u>on the same Cross Row</u> as the +ive power jumper lead
- Push other Resistor leg into a Cross-Row several rows down on the same side of the Board
- Insert LED <u>LED needs correct polarity</u> +ive leg is longer; –ive has 'flat spot' in coloured plastic
- Push +ive LED leg into a hole <u>on the same +ive Cross Row</u> as the Resistor leg
- Push -ive LED leg into a hole <u>on the same -ive Cross Row</u> as the -ive power Jumper lead spanning the gap in the Breadboard
- Light Globe will light.... if not. Check the line of 'power' does it flow from one line to the next? Is it a complete 'loop'? Are the jumper ends and the LED legs all correct Cross-rows?
- Current must be flowing in a complete 'loop' or else the LED will not light
- What is demonstrated? When Resistor is placed in Series with an LED (with correct polarity) LED will light. Resistors are inserted either way [Resistor ends are <u>not +ive or -ive</u> polarity]
- Substitute a 1,000 ohm [brown, black, red] Resistor LED still lights, but not as bright.
- Conclusion; Using a Resistor three times the value of the initial 330 ohm one, the LED is
 reasonably bright. Using Resistors of much higher value? LED would still light, but much dimmer.

Image 5. See "Note 2"– Reduce Voltage to Protect LED

Demo 6. Turning a circuit into a simple Continuity Tester	
	• To test 'continuity' by making TWO Test Leads - Resistor & LED from Demo5, remain in the circuit
	9v battery leads are attached to the Breadboard +ive & -ive rails
	• +ive jumper lead has one end in the Red +ive rail line & other end in same Cross-Row as Resistor
a b c d 6 a a a a a a a a a a a a a a a a a a a	leg
	Remove one end of the -ive jumper lead that was attached to -ive LED leg - remove the end from
	the Cross-Row – leave other end in the Blue –ive rail. One end of jumper is free of the board – this is
	now a crude Test Lead
	Use ANOTHER jumper lead to make the other Test Lead
	 Insert a jumper into where the first lead was removed from the -ive jumper lead connection –
	• Check the Breadboard circuit chould be usive rail to usive jumper, through resister, through LED to a
	Test Lead
	 Other side of boardive rail to a -ive Test lead - LED is not lit - nower loop is NOT complete until
	'something' joins these two test leads
	 When the two Test Leads are touched together, the LED will light – that is a Continuity Test
Image 6	• Test for continuity in other metals ie touch them on pieces of metal, or another jumper lead, to
See "Note 3" Effect of Corrosion on Conductors	show that metallic materials conductor electricity.
	See "Notes 3 Effect of Corrosion on Metal Conductors
Notes	<u>1.</u> How is a Breadboard constructed?
	Note "Red +" and "Blue –" long Rails/Rows.
	All holes along the Red rail are connected.
	All the holes along the Blue Rail are connected.
	Look at the shorter 'Cross-Rows'. All holes in each short Row are connected.
	The board is split in TWO long-ways.
on Components	It can be 2 separate boards or you can 'jumper' across and make it ONE board.
and steps	Connecting a 9V battery: Attach battery cap to battery & insert the red battery lead into a noie in the
	Insert Black battery lead in a hole in the Blue -ve rail [any hole in the long row – now All holes in that
	rail have -ive power. 'Negative' is also called 'Ground' or be marked GND in circuits or diagrams.
	A complete loop of power is required for a current to flowing and as components like lights or buzzers
	are added they must all be connected within the 'loop' or the circuit will not work.
	You notice the board soon becomes jumbled & it's a tight fit for fingers.
	This is why we expand across to the 'other side' of the breadboard.
	Spread projects out so you can see the flow of components but remember
	IF you use the Other side of the board you must "join the two short cross rows" to make it <u>one board</u> .

